



ADITYA UNIVERSITY

A Case Study Report

On

Design of a 3-Bit Synchronous Counter for Digital Timers

In the course

**Digital Logic Design
(2501EC95)**

In

B. Tech I Year I Sem


Submitted by

K Shalini

25B11CS477

Faculty Signature

1. Introduction

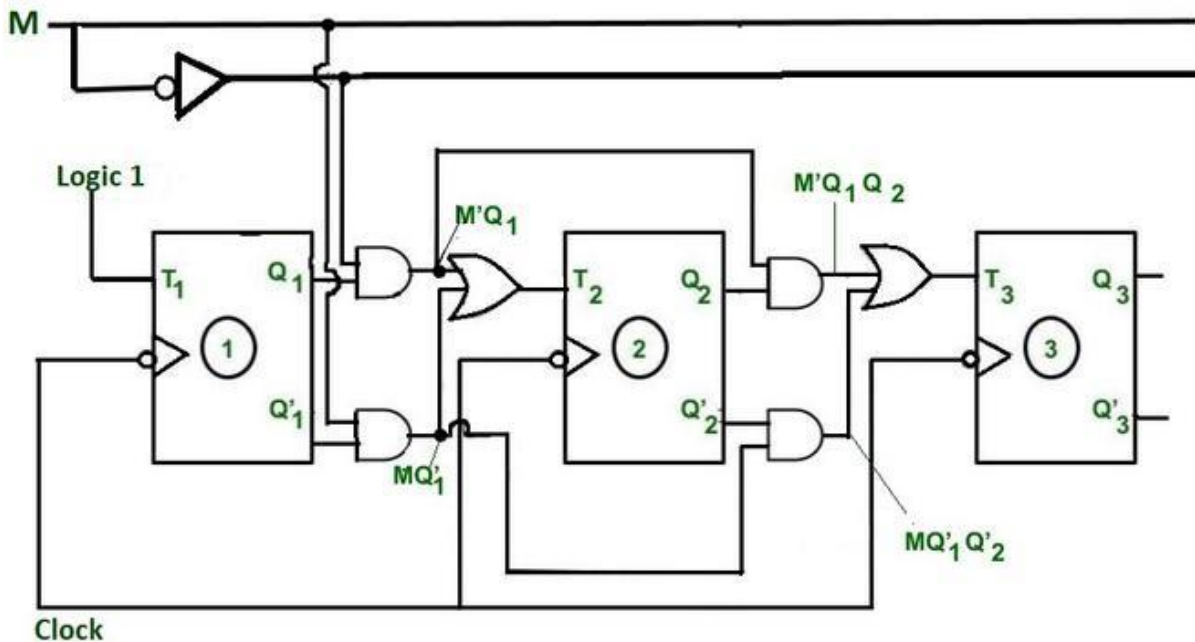

Digital timers are widely used in electronic devices such as clocks, stopwatches, microwave ovens, and industrial controllers. A fundamental building block of these systems is a counter, which keeps track of time by counting clock pulses.

This case study focuses on the design of a 3-bit synchronous counter, emphasizing synchronous operation for accuracy, reliability, and ease of control.

2. Problem Statement

The objective of this case study is to design a 3-bit synchronous binary counter that:

- Counts from 000 to 111 (0 to 7) in binary
- Updates all flip-flops simultaneously using a common clock
- Can be used as a basic module in digital timer applications
- Demonstrates predictable and stable operation

2. Background and Theory

3.1 Counter

A counter is a sequential digital circuit that goes through a prescribed sequence of states upon the application of clock pulses.

3.2 Synchronous Counter

In a synchronous counter:

- All flip-flops are triggered by the same clock signal
- State changes occur simultaneously
- Delay problems common in asynchronous counters are avoided

3.3 Flip-Flop Selection

For this design, JK flip-flops are used due to their versatility and toggling capability.

4. Design Specifications

Parameter	Description
Counter Type	Synchronous Binary Counter
Number of Bits	3
Maximum Count	7 (111)
Flip-Flops Used	JK Flip-Flops
Clock	Common clock input
Application	Digital Timers

5. State Diagram

The counter follows the sequence:

000 → 001 → 010 → 011 → 100 → 101 → 110 → 111 → 000

This cyclic sequence repeats continuously with each clock pulse.

M	Q ₃	Q ₂	Q ₁	Q ₃ [*]	Q ₂ [*]	Q ₁ [*]	T ₃	T ₂	T ₁
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	0	1	0	0	0	1

7. Logic Design

7.1 Flip-Flop Input Conditions

- Flip-Flop Q0
 - Toggles at every clock pulse
 - J0 = 1, K0 = 1
- Flip-Flop Q1

- Toggles when $Q_0 = 1$
- $J_1 = Q_0, K_1 = Q_0$
- Flip-Flop Q_2
 - Toggles when $Q_0 \text{ AND } Q_1 = 1$
 - $J_2 = Q_0 \cdot Q_1, K_2 = Q_0 \cdot Q_1$

8. Block Diagram Description

The circuit consists of:

- Three JK flip-flops connected in parallel to a common clock
- Logic gates (AND gates) to generate toggle conditions
- Outputs Q_0, Q_1 , and Q_2 forming the 3-bit binary count

9. Application in Digital Timers

In digital timers:

- The 3-bit synchronous counter can represent seconds or minutes
- It provides accurate timing due to synchronized operation
- Multiple counters can be cascaded to form higher-bit timers

10. Advantages of Synchronous Counter

- Reduced propagation delay
- Improved speed and reliability
- Easier timing analysis
- Suitable for high-frequency applications

11. Conclusion

This case study presented the design and operation of a 3-bit synchronous counter used in digital timers. By employing synchronous design principles and JK flip-flops, the counter achieves reliable and predictable performance. Such counters serve as essential components in modern digital systems and timing applications.

